 



Lab 9 [Extra Credit]: 4b adder using a simple half-adder

Today's lab is about developing Verilog modules for a 4b adder using a simple half-adder cell as building block. First we will write a Verilog module for a half adder and verify its functionality with test bench simulations. Then using that half-adder module, we will write the full-adder cell and verify its functionality with test bench simulations. Finally using that full adder module, we write the Verilog module for a 4b adder and verify its functionality. Before we write the modules, we need to understand how half adder and full adder works. When creating an adder, we have to design the incremental sub-systems in way that it can be re-used like using half adder to create full adder. This technique reduces the design effort, cost and minimizes the difficulty of troubleshooting. Half Adder computes the sum, S and carry out, C from its two input A and B. It is different from a Full adder because it doesn't take the carry-in bit into account. So for half adder the possible inputs are - $0+0 = 0$ (0 is sum), $0+1 = 1$, $1+0 = 1$, and $1+1 = 10$ (1 is Carry). As we can see, it only takes 2 inputs A, B so $2^2 = 4$ possible combinations.




Next is Full Adder, it is a circuit that produces a sum and carry out like half adder but also considers the carry-in as input. So it has three inputs in total - A, B and Cin, so $2^3 = 8$ possible

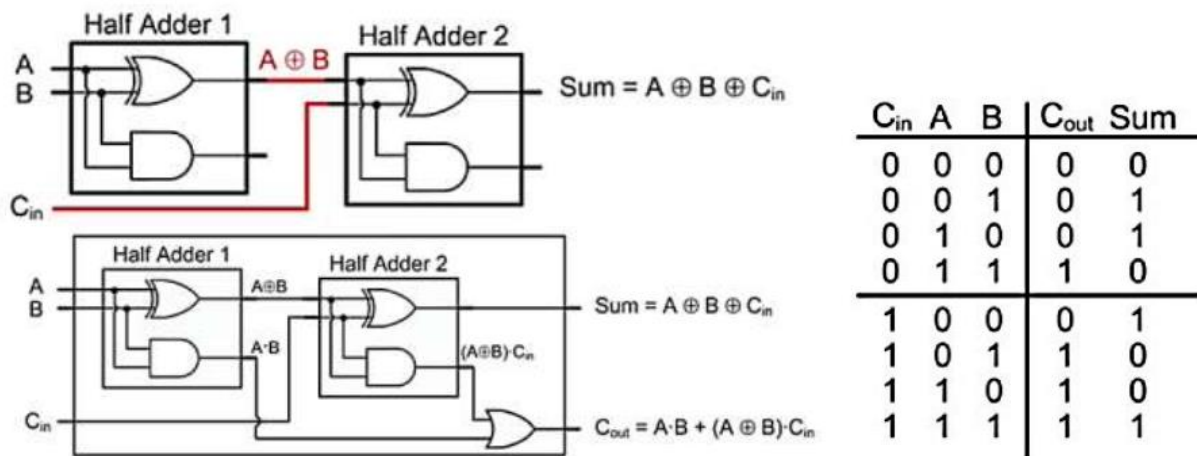combinations. We can create a full adder by combining two half adder, where the first adder will take the A & B input, and the second half adder will take the sum from first HA and C_{in} as the input. So we have a sum and C_{out} (added two C_{out} from each HA) in the end for output.




Now we can use the full adder to create multibit adder, in this case we will create a 4b adder that will uses 4 full adder. In a full adder, we have a sum and a carry out for each bit position. So in multi-bit adder, the carry out of each full adder is used as the carry in for the next significant bit. That's why each subsequent full adder needs to wait for the carry to be produced by the previous stage. So, the carry is said to 'ripple through' the circuit and 4b adder is using this Ripple Carry Adder architecture.

 


Now we can write the modules for each - half adder, full adder and a 4b adder. For half adder, we have inputs A, B and output sum and Cout. From the circuit we can see it has a XOR gate for sum and an AND gate for Cout with A, B input. So we can write it as - assign $\text{sum} = A \oplus B$ (^ is XOR) and assign $\text{Cout} = A \& B$. That's our module for HA and for testbench we have to try out all possible combinations. In testbench we will have reg A, B and wire as SUM and Cout. We need a reg 2 bit value that using which we can assign values to A and B. Next, we will create a half adder dut and map all the inputs and outputs. After that we will declare a integer i (32 bit). Now using for loop, we have to try all 4 combinations and we can do it by assigning $\{\text{value}\} = i$ which will take the two MSB (since value is 2 bit) and make $A \leq \text{value}[0]$ and $B \leq \text{value}[1]$. This will try out all combinations and we have #15 nanoseconds delay for each cycle. After verifying this using simulation waveforms, we can start with Full adder module. For Full adder, wire S1, C1, C2 to connect the two half adder outputs inside the module. Then we will create two half adder, where we will have output S1 and C1 from the first HA, and the second HA will take S1 as input and will output sum and C2. Next we have to add Cout's from each HA, and we can do that by assigning $\text{Cout} = C1 + C2$. Then we will create a testbench for this FA similar to HA but we have to make some changes considering the circuit and new Cin as input. For Cin, we will have a reg Cin and the reg value will now be 3 bit because we have 3 inputs. Next, same as before we will create a half adder and for the loop, now $i < 8$ because we have $2^3 = 8$ total combinations. Inside the for loop we have to assign the value for $\text{Cin} \leq \text{value}[2]$ along with A and B. Everything will stay the same and this concludes the testbench for Full adder. After running the simulation and verifying it, we can start with 4b adder. For the 4b module, we will have input A (4 bits), B(4 Bits), Cin and for output we will have sum (4 bit) and a Cout.

Then based on the circuit, we need 3 wires - C1, C2, C3 that will be connected to each full adder. Next we will create 4 full adder and assign the input and output sequence based on the Fig. 3 circuit. For the testbench, we will have 4 bit reg A, 4 bit reg B, Cin assigned to 0 initially, wire 4 bit sum, wire cout and reg of 8 bit value. We need 8 bits because each full adder takes 2 bits so $4 \times 2 = 8$ bits in total. Then we will create a fourbitadder and for the loop, now $i < 256$ because we have $2^8 = 256$ total combinations. Inside the for loop we will assign the A value to first 4 MSB and B to next 4 MSB. This will try out all possible combinations for the testbench and if we run the simulation we get the following waveforms -

 

Waveform Verification -

 To verify 4b adder works, we can try adding the values from the waveforms and see if we get the same sum and Cout. In the following waveform:



For the next waveform, we have A = 0010 and B = 1101 (yellow line). If we add A + B we get sum = 1111 and cout as 0. We get the same values from the waveforms for sum = 1111 and cout = 0. Trying out all this addition examples verifies that 4b adder functionality works and the code for



each half-adder, full-adder, 4b adder including the testbenches are attached.